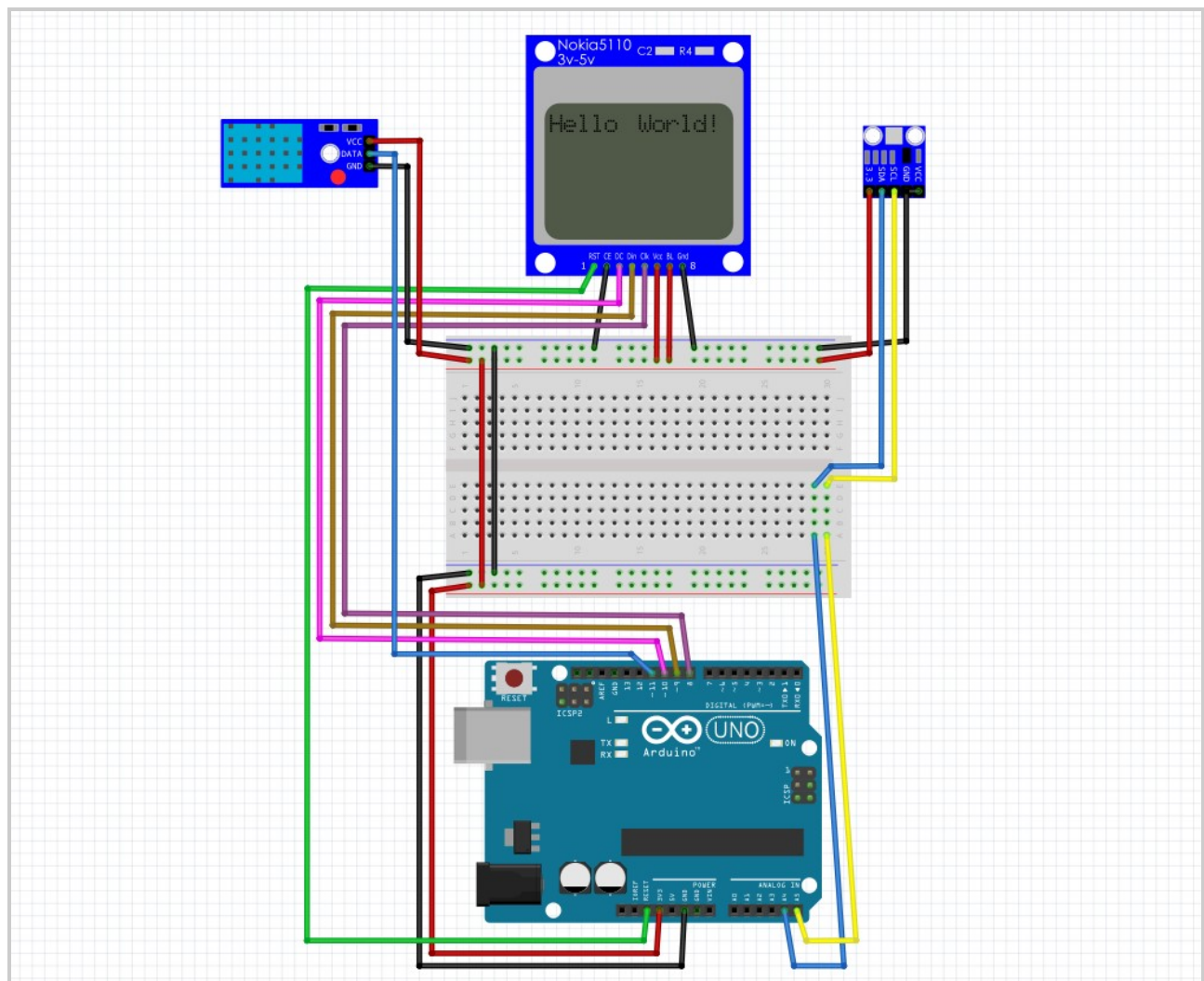


COMPLETE CIRCUIT

Here is what the complete circuit should look like:



MARK
INCOMPLETE

CONTINUE →

MARK
INCOMPLETE

CONTINUE →